

### 13 DC Circuits – Capacitors

$$Q = CV$$

$$C_{\text{eq, parallel}} = \sum_i C_i$$


$$C_{\text{eq, series}}^{-1} = \sum_i C_i^{-1}$$

$$C_{\text{plate}} = \epsilon_0 \frac{A}{d}$$


$$C_{\text{dielectric}} = \kappa C_0$$

$$U = \frac{1}{2} CV^2 = \frac{Q^2}{2C} = \frac{1}{2} QV$$

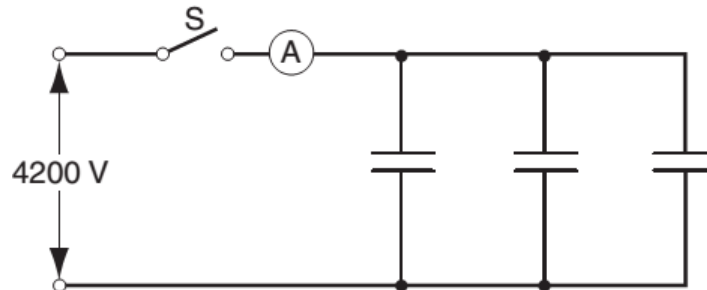
1. (RHK Exercise 30-12) Each of the uncharged capacitors in the figure below has a capacitance of  $25 \mu\text{F}$ . A potential difference of  $4200 \text{ V}$  is established when the switch  $S$  is closed. How much charge then passes through the ammeter  $A$ ?



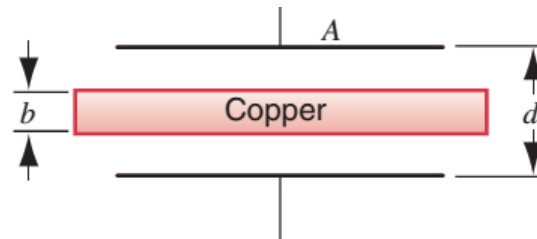
2. (RHK Exercise 30-37) A slab of copper of thickness  $b$  is thrust into a parallel-plate capacitor as shown below. (a) What is the capacitance after the slab is introduced? (b) If a charge  $q$  is maintained on the plates, find the ratio of stored energy before / after the slab is introduced. (c) How much work is done on the slab as it is inserted? Is the slab pulled in or do you have to push it in? (d) What changes if the potential  $\Delta V$  is held fixed, instead of  $q$ ?



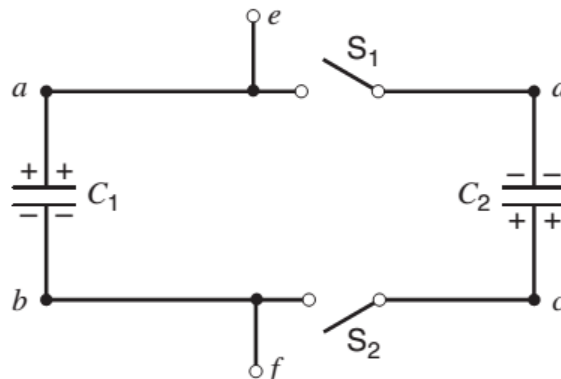
3. (RHK Problem 30-5) In the figure below, capacitors  $C_1 = 1 \mu\text{F}$  and  $C_2 = 3 \mu\text{F}$  are each charged to a potential difference  $\Delta V = 6 \text{ V}$ , but with opposite polarity, so that points  $a$  and  $c$  in the figure are on the positively charged side, and points  $b$  and  $d$  are on the negative side. After closing switches  $S_1$  and  $S_2$ : (a) What is the potential difference between points  $e$  and  $f$ ? (b) What is the charge on  $C_1$ ? (c) What is the charge on  $C_2$ ?



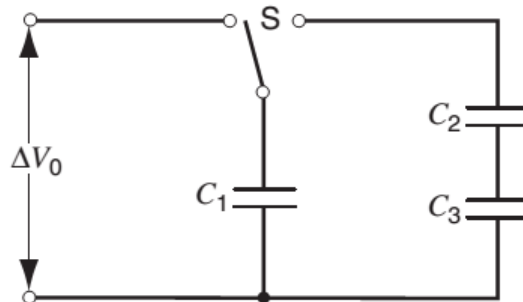4. (RHK Problem 30-6) When switch S is thrown to the left in the circuit below, the plates of the capacitor  $C_1$  acquire a potential difference  $\Delta V_0$ . The other capacitors  $C_2$  and  $C_3$  are initially uncharged. The switch is now thrown to the right. What are the final charges  $q_1, q_2, q_3$  on the corresponding capacitors?



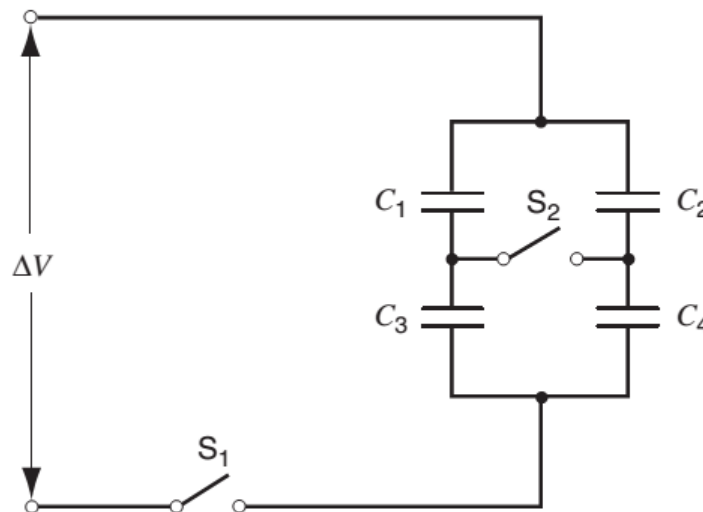5. (RHK Problem 30-9) In the circuit below, a battery supplies a potential difference of  $\Delta V = 12V$ . (a) Find the charge on each capacitor when the switch  $S_1$  is closed and (b) when (later) switch  $S_2$  is also closed. Take  $C_1 = 1 \mu F$ ,  $C_2 = 2 \mu F$ ,  $C_3 = 3 \mu F$  and  $C_4 = 4 \mu F$ .



6. (RHK Problem 30-10) Find the equivalent capacitance between points  $x$  and  $y$  in the circuit below. Assume that  $C_1 = C_3 = C_4 = C_5 \equiv C$ , but  $C_2 \neq C$ . (Hint: Apply a potential difference  $\Delta V$  between  $x$  and  $y$  and write down all the relationships that involve the charges and potential differences for the separate capacitors.)

